

Class Activity 4: Designing Sequential Circuits with JK Flip-Flops

 


Figure. JK Flip-Flop

Task 1: Design the Sequential Circuit

1. State Diagram Analysis:

- Draw and analyze the state diagram for the JK Flip Flop.

2. State Table:

- Create the state table based on the state diagram.

3. Circuit Diagram:

- Draw the complete circuit diagram including the JK flip-flops and combinational logic.

Task 2: Simulate the Circuit

1. VHDL Code:

- Write the VHDL code for the designed sequential circuit.
- Include the JK flip-flop components and the combinational logic.

2. Testbench:

- Create a testbench to simulate the circuit.
- Include test cases that cover all state transitions.

3. Simulation:

- Use EDA Playground to simulate the VHDL code.

Materials Needed:

- EDA Playground access
- VHDL code templates
- Printed handouts of the state diagram and state table

Hints:

1. Refer to the JK flip-flop excitation table to determine the J and K inputs.
2. Use EDA Playground to write, simulate, and verify your VHDL code.